



École nationale supérieure en systèmes avancés et réseaux

Report SE520

Subject: Implementation of RSA on FPGA

Minh Quang Nguyen

Bessem BEN AMOR

5A EIS & Mistre

I. Introduction

The goal of this lab is to implement the RSA encryption and decryption algorithm on a Basys-3 FPGA board. The work includes RTL and circuit designs of the arithmetic modules involved in the 16-bit RSA computations, representing encrypted and decrypted message with 7-segment display on FPGA, and analysis of brute-force attack on the private key used for the encryption process.

II. Lab code and result

1. Mod m adder

1.1. Behavioral description

modm_addition.vhd

```
architecture rtl of modm_addition is
begin
    process(x,y)
        variable z1, z2 : integer;
        variable c1, c2 : integer;
        variable L : line;
    begin
        z1 := to_integer(unsigned('0'&x) + unsigned(y));
        z2 := (z1 mod 2**k) + (2**k - to_integer(unsigned(m))); --- to be completed!
        c1 := z1/2**k;
        c2 := z2/2**k; --- to be completed!

        if c1 = 0 and c2 = 0 then
            z <= std_logic_vector(to_unsigned(z1 mod 2**k, k)); --- to be completed!
        else
            z <= std_logic_vector(to_unsigned(z2 mod 2**k, k)); --- to be completed!
        end if;
    end process;
end;
```

modm_adder.vhd

```
architecture rtl of modm_adder is
    signal long_x, sum1, long_z1, sum2: std_logic_vector(k downto 0);
    signal c1, c2, sel: std_logic;
    signal z1, z2: std_logic_vector(k-1 downto 0);
    --constant minus_m: std_logic_vector(k-1 downto 0) := std_logic_vector( - signed(m));
    signal minus_m: std_logic_vector(k-1 downto 0);


begin
    long_x <= '0' & x;
    sum1 <= std_logic_vector(unsigned(long_x) + unsigned(y));
    c1 <= sum1(k);
    z1 <= sum1(k-1 downto 0);
    minus_m <= std_logic_vector( - signed(m));
    --- to be completed!
    long_z1 <= '0' & z1;
    sum2 <= std_logic_vector( unsigned(long_z1) + to_unsigned((2**k + to_integer(unsigned(minus_m))),k));
    c2 <= sum2(k);
    z2 <= sum2(k-1 downto 0);
end;
```

Datapath by completing

The algorithm performs addition between two integers, x and y , with modulo m , and k representing the number of bits.


- $z1 = x + y$
- $z2 = z1 \bmod 2^k + 2^k - m$

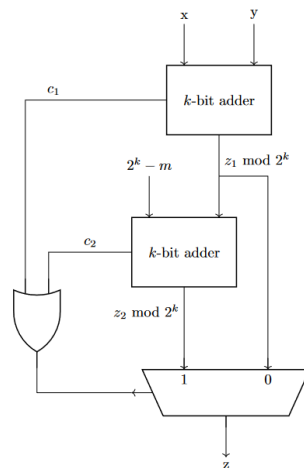The result will be equal to : $z2 \bmod 2^k$ if $[(z1 \geq m) \text{ or } (z2 \geq m)]$,
Otherwise, it will be $z1 \bmod 2^k$.




 Example :


In this simulation, when we input $x = 129$ and $y = 105$ with $m = 239$, with $k=8$.
we obtain the following result:



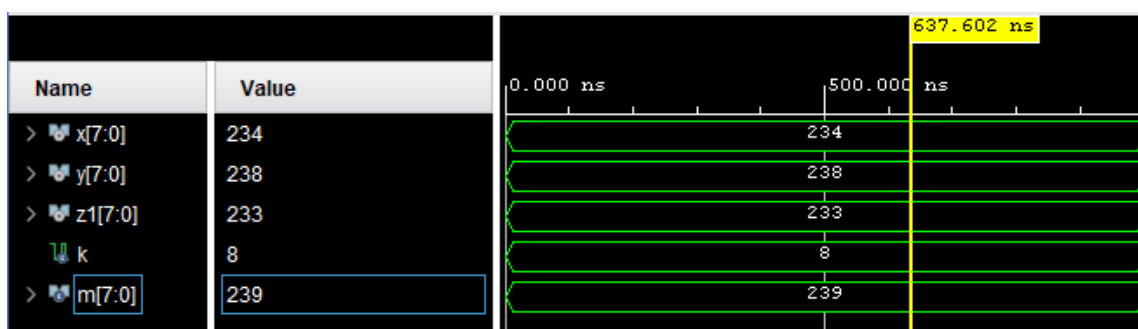Another example with : $x = 234$, $y = 238$



Also for modm_adder with x=215, y =35

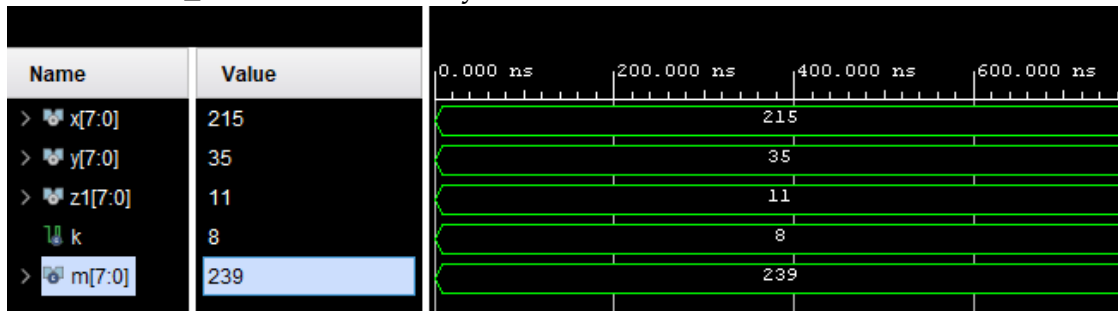

2. Modulo m multiplier

2.1. Finite State Machine :

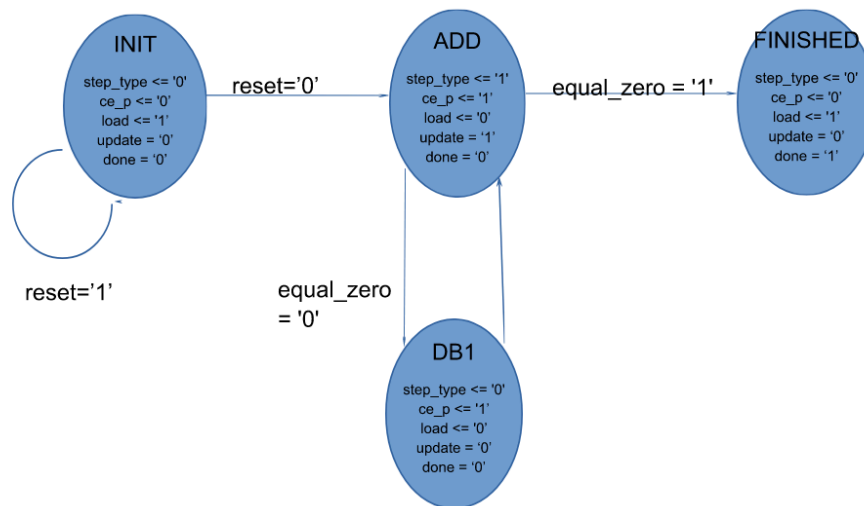


Figure x: FSM

2.2. testbench modm_multiplier.vhd

tb_modm_multiplier.vhd


```

clk_process :process
begin
  clk <= '0';
  wait for clk_period;
  clk <= '1';
  wait for clk_period;
end process;

stim_proc: process
begin
  reset <= '1';
  wait for 20ns;
  reset <= '0';
  x <= std_logic_vector(to_unsigned(235, k));
  y <= std_logic_vector(to_unsigned(10, k));
  wait for 1000 ns;

  wait;
end process;
  
```

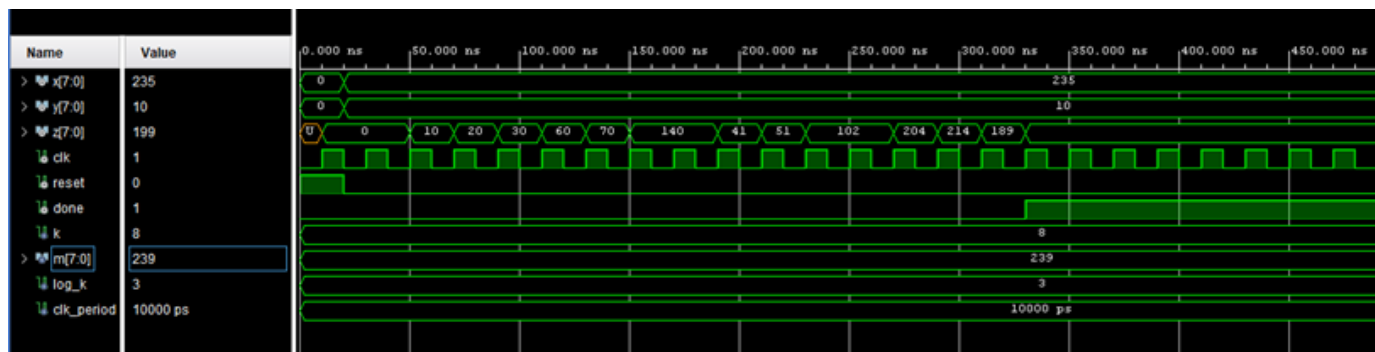In this simulation of the testbench with inputs : x=235, y=10 and k=8.



2.3. Computation time

As showing the simulation in 2.3


Computation time analysis = $2k-1$

Comment: because $2*(k-1)$ cycles for ADD => DB1, then 1 cycle for the last add

Check : $k = 8$, time = 15 cycles => correct

3. Modulo m exponentiation

3.1. FSM for the modulo m exponentiation

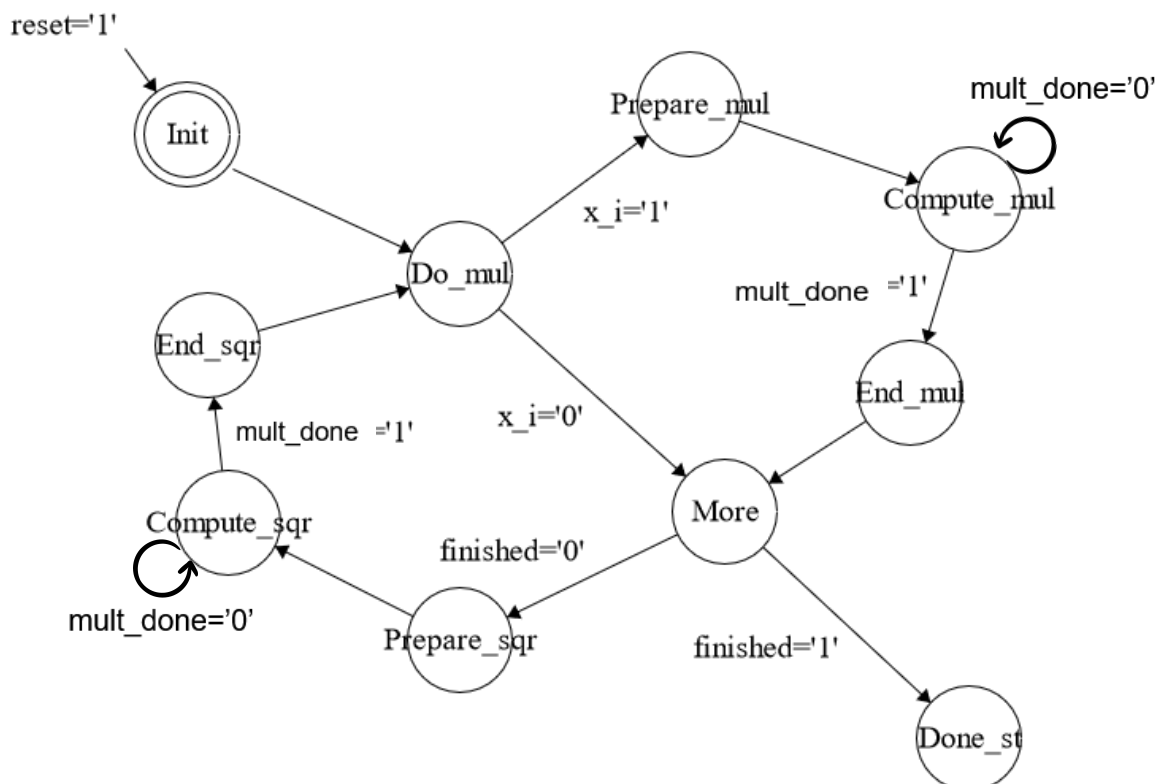

3.2. output values of the FSM

```

fsm_output: process(current_state)
begin
  case current_state is
    when Init
      => save <='0'; update <='0' ; step_type <='0'; load <='1' ; done <='0'; mult_reset <='0' ;
    when Do_mul
      => save <='0'; update <='0' ; step_type <='0'; load <='0' ; done <='0'; mult_reset <='1' ;
    when Prepare_mul
      => save <='0'; update <='0' ; step_type <='1'; load <='0' ; done <='0'; mult_reset <='0' ;
    when Compute_mul
      => save <='0'; update <='0' ; step_type <='1'; load <='0' ; done <='0'; mult_reset <='0' ;
    when End_mul
      => save <='1'; update <='0' ; step_type <='1'; load <='0' ; done <='0'; mult_reset <='0' ;
    when Prepare_sqr
      => save <='0'; update <='0' ; step_type <='0'; load <='0' ; done <='0'; mult_reset <='0' ;
    when Compute_sqr
      => save <='0'; update <='0' ; step_type <='0'; load <='0' ; done <='0'; mult_reset <='0' ;
    when End_sqr
      => save <='1'; update <='0' ; step_type <='0'; load <='0' ; done <='0'; mult_reset <='0' ;
    when More
      => save <='0'; update <='1' ; step_type <='0'; load <='0' ; done <='0'; mult_reset <='1' ;
    when Done_st
      => save <='0'; update <='0' ; step_type <='0'; load <='0' ; done <='1'; mult_reset <='1' ;
  end case;
end process fsm_output;

```

3.3. Design code, testbench and simulation

```


m <= std_logic_vector(to_unsigned(219, k));
x <= std_logic_vector(to_unsigned(6, k));
y <= std_logic_vector(to_unsigned(6, k));

wait until done = '1';

reset <= '1' ;
wait for 20 ns ;
reset <= '0' ;
wait for 10 ns ;

m <= std_logic_vector(to_unsigned(219, k));
x <= std_logic_vector(to_unsigned(8, k));
y <= std_logic_vector(to_unsigned(2, k));


```

 

```

m <= std_logic_vector(to_unsigned(65535, k));
x <= std_logic_vector(to_unsigned(65535, k));
y <= std_logic_vector(to_unsigned(65535, k));

```

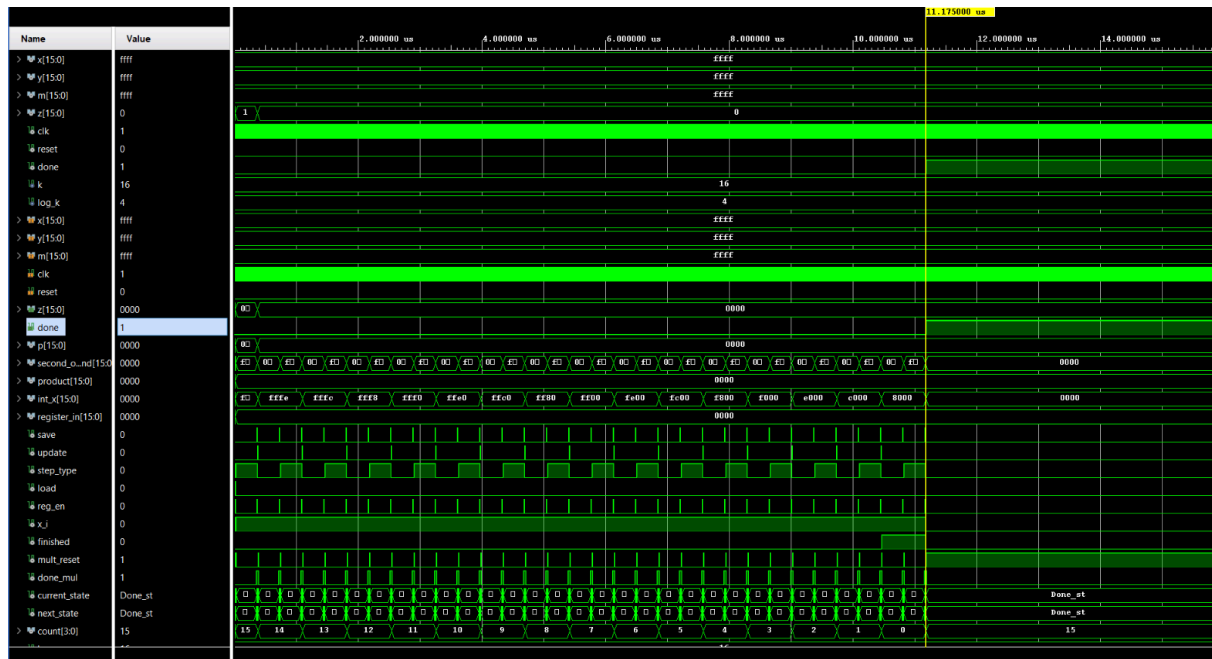

3.4. Big number

```

constant k: integer := 192;
constant log_k: integer := 58;

constant m : std_logic_vector(k-1 downto 0) := (191 downto 17 => '1', 15 downto 0 => '1', others => '0');


signal x, y, z: std_logic_vector(k-1 downto 0);
signal clk, reset, done: std_logic := '0';
signal stage: std_logic_vector(3 downto 0);

-- Stimulus process
stim_proc: process
begin

    reset <= '1';
    wait for 10 ns ;
    reset <= '0';
    -- (2^k*192)-1-(2^k*16)
    x <= m;
    y <= (190 downto 0 => '1', others => '0');
    wait until done = '1';
    wait;
end process stim_proc;

```

 From the waveform, we can see $z = y$ as desired



3.5. Compute worst-case execution time

* Computational time is only dependent on k and x , while m and y do not pose an impact.

* We start the exponential computation at 15ns. Clock cycle is 10ns.

* Improved code, so each mul only takes **2k cycles**, 2k-1 for the multiplier module to output done, and 1 cycle lag for the exponential function to take the done input and move on to the next state.

```
fsm_output: process(current_state)
begin
  case current_state is
    when Init => save <= '0'; update <= '0'; step_type <= '0'; load <= '1'; done <= '0'; mult_reset <= '0';
    when Do_mul => save <= '0'; update <= '0'; step_type <= '0'; load <= '0'; done <= '0'; mult_reset <= '1';
    when Prepare_mul => save <= '0'; update <= '0'; step_type <= '1'; load <= '0'; done <= '0'; mult_reset <= '0';
    when Compute_mul => save <= '0'; update <= '0'; step_type <= '1'; load <= '0'; done <= '0'; mult_reset <= '0';
    when End_mul => save <= '1'; update <= '0'; step_type <= '1'; load <= '0'; done <= '0'; mult_reset <= '0';
    when Prepare_sqr => save <= '0'; update <= '0'; step_type <= '0'; load <= '0'; done <= '0'; mult_reset <= '0';
    when Compute_sqr => save <= '0'; update <= '0'; step_type <= '0'; load <= '0'; done <= '0'; mult_reset <= '0';
    when End_sqr => save <= '1'; update <= '0'; step_type <= '0'; load <= '0'; done <= '0'; mult_reset <= '0';
    when More => save <= '0'; update <= '1'; step_type <= '0'; load <= '0'; done <= '0'; mult_reset <= '1';
    when Done_st => save <= '0'; update <= '0'; step_type <= '0'; load <= '0'; done <= '1'; mult_reset <= '1';
  end case;
```

* Since $x = 11 \dots 11$, mul is always executed for each bit position, thus 2k cycles for the computation, and 2 for prepare and compute stage. Total mul = $k \cdot (2k+2)$

* Since square is executed (k-1) times, 2k cycles for the computation, and 2 for prepare and compute stage. Total square = $(k-1) \cdot (2k+2)$


* Transition between mul and square, take $(k-1) + (k) - 1 = 2k-2$ cycles

* Ending takes 2 cycles

* Thus total = $(2k-1)(2k+2) + 2k = 4k^2 + 4k - 2$


Verify with examples:

 a) $x = 255$, $k = 8$. Cycles = $4k^2 + 4k - 2 = 286 = (2875\text{ns} - 15\text{ns}) : 10\text{ns}$




 
b) $x = 0\text{xFFF}\dots\text{FF}$, $k = 192$. Cycles = $4k^2 + 4k - 2 = 148222$

From waveform = $1482220 : 10 = 148222 \rightarrow$ correct



4. RSA in the Basys 3

4.1. RSA encryption and decryption

  

In the constraints file we have declared sw1 to be V17, and sw2 to be V16 of Basys 3

When sw1=0, sw2=1 => encrypting the cleartext to ciphertext F20F using public key

When sw1=0, sw2=1 => decrypting the ciphertext to cleartext 8000 using private key

```

signal cleartext : std_logic_vector(15 downto 0) := "1000000000000000"; --0x8000
signal cryptotext : std_logic_vector(15 downto 0) := x"F20F";
signal priv_k : std_logic_vector(15 downto 0) := x"D4BF";
signal publ_k : std_logic_vector(15 downto 0) := x"007F";
signal n : std_logic_vector(15 downto 0) := x"F797";
signal x,y,z : std_logic_vector(15 downto 0);
begin

x <= priv_k when sw2 = '0' else publ_k;
y <= cleartext when sw1 = '0' else cryptotext;

Display_inst : display
port map (
    clk          => clk,
    seg          => seg,
    dp           => dp,
    an           => an,
    hex2led_int1 => z(3 downto 0),
    hex2led_int2 => z(7 downto 4),
    hex2led_int3 => z(11 downto 8),
    hex2led_int4 => z(15 downto 12)
);

-- Instantiate the modm_exponentiation entity
ModExp_inst : modm_exponentiation
generic map (
    k => 16,
    log_k => 4
)
port map (
    x => x,
    y => y,
    m => n,
    clk => clk,
    reset => btn,
    z => z,
    done => led
);


```

4.2. Brute-force attack

We have made the datapath and FSM diagram of the scheme. Unfortunately, we have not realized this logic on board.

The datapath consists of the RSA module from 4.1, a comparator to compare the cleartext with decrypted message produced by the bruteforce attack from the RSA. If there is a match, we alert the controller to output this value.

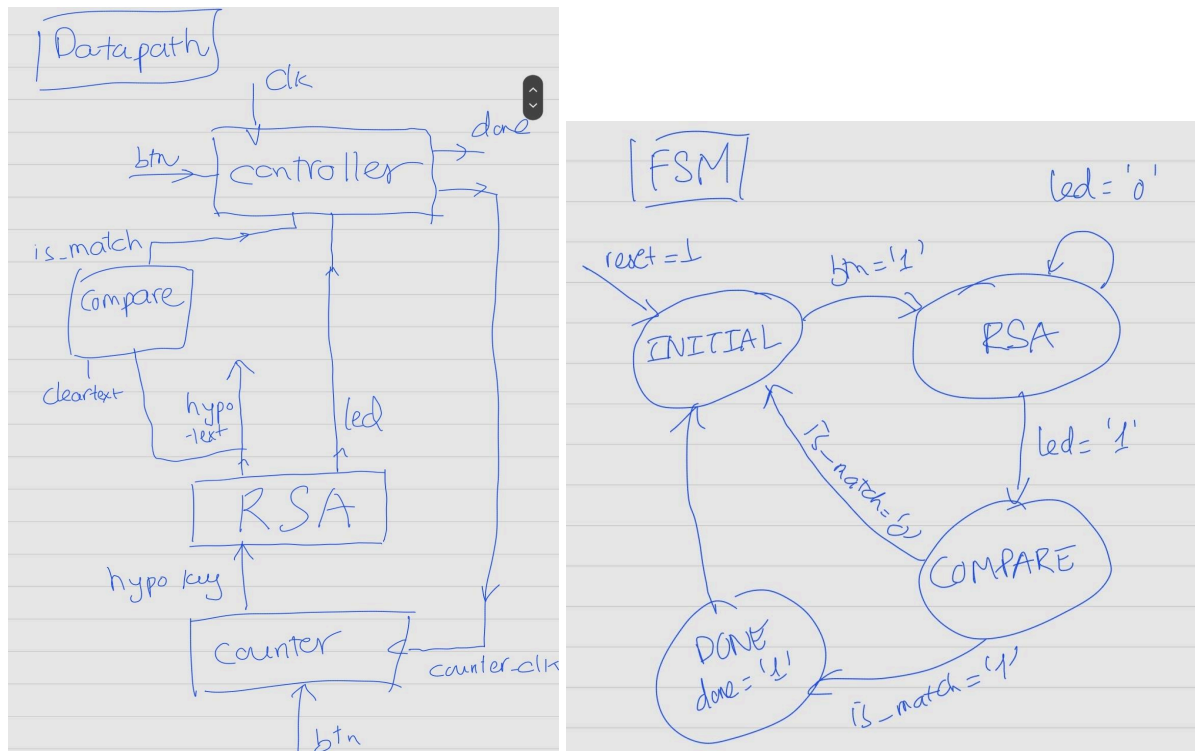From the FSM, we can see our design could continue to output different “matching” private keys as button btn are being pressed. Only if there is a match that the output is displayed.



III. Conclusion

Through the lab, we have gained hands-on experience in implementing RSA encryption and decryption logic on FPGA. We have also gained insights in designing VHDL modules and testing them throughout. Lastly, we learned about the difficulty and feasibility of brute-force attack on this RSA implementation.